

Quantum Random Access Memory



CPSC 4470/5470

Introduction to Quantum Computing


Instructor: Prof. **Yongshan Ding**

Computer Science, Applied Physics, Yale Quantum Institute

Implementing General-Purpose Oracles

Select Operator:

$$O_f = \prod_{x \in \{0,1\}^n} |x\rangle\langle x| \otimes X^{f(x)}$$

 

Implementations:

1. Sequential Query Circuit:

- Gates: Toffoli, CX gates
- Time: $O(N)$
- Qubits: $\log N$ address qubits, 1 bus qubit, 1 ancilla qubit.

2. Fanout QRAM:


- Gates: Fanout, cSWAP gates
- Time: $O(\log N)$
- Qubits: $\log N$ address qubits, 1 bus qubit, $O(N)$ ancilla qubits.

3. Bucket-Brigade QRAM:

- Gates: cSWAP gates
- Time: $O(\log N)$
- Qubits: $\log N$ address qubits, 1 bus qubit, $O(N)$ ancilla qubits.

Sequential Query Circuit

 
Implement $O(N)$ **multi-controlled-NOT** gates one at a time.



Implementing a Multi-Controlled-NOT Gate

Using Toffoli gates (acting on three qubits) and few ancillary qubits.


Example: $\Lambda_5(X)$ gate

 

$\Rightarrow$

Using multiple $\Lambda_3(X)$ gates?

Dirty Ancilla $|a\rangle$:

 

$$\text{AND}_5(x_0, x_1, x_2, x_3, x_4) = \text{AND}_3(\text{AND}_3(x_0, x_2, x_4), x_1, x_3)$$

What's the resulting state (including ancilla)?


"Uncompute" to reset ancilla to initial state.

What if the initial ancilla state is unknown ("dirty")?

Write to output based on "toggling" ancilla state.

Implementing a Multi-Controlled-NOT Gate

 
Using Toffoli gates (acting on three qubits) and few ancillary qubits.



$$\text{AND}_3(x_0, x_2, x_4) = \text{AND}_2(\text{AND}_2(x_0, x_2), x_4)$$

Implementing a Multi-Controlled-NOT Gate

 Using Toffoli gates (acting on three qubits) and few ancillary qubits.




For $\Lambda_n(X)$ gate, we can implement using $\approx 16n$ Toffoli gates. **Total timesteps:** $O(n)$.

Implementing a Multi-Controlled-NOT Gate

Using Toffoli gates (acting on three qubits) and few ancillary qubits.

$\Lambda_n(X)$ gates

 

$\Rightarrow$

Implement AND_n using AND_2 gates and ancilla (qu)bits?

- We just saw: $O(n)$ -size, $O(n)$ -depth circuit with 1 ancilla.

$$\text{AND}_n(x_0, \dots, x_{n-1}) = \text{AND}_{\lceil n/2 \rceil}(\underbrace{\text{AND}_{\lceil n/2 \rceil}(x_{i:\text{even}}), x_{i:\text{odd}}}_{\text{AND}_2(\dots, \text{AND}_2(\text{AND}_2(x_0, x_2), x_4))})$$

Can we do better?

- **Logarithmic depth:** $O(n)$ -size, $O(\log n)$ -depth circuit with $O(n)$ ancilla.


Binary tree of AND functions.

- **Constant depth:** $O(n)$ -size, $O(1)$ -depth **dynamic** circuit with $O(n \log n)$ ancilla.

Dynamic circuit: mid-circuit measurement and feedforward.

Sequential Query Circuit

 Implement $O(N)$ **multi-controlled-NOT** gates one at a time.



Each multi-controlled-NOT gate takes $O(n)$ time steps. What is the **total depth** for arbitrary $f(x)$?


Quantum Multiplexer

Multiplexing Operator ($N = 2^n$):

$$\text{MUX}_N = \prod_{x \in \{0,1\}^n} |x\rangle\langle x| \otimes U_x$$


If **select qubits** are $|x\rangle$:
apply U_x to the **output qubit**.

Quantum Switch (MUX_2):


 


$$|0\rangle\langle 0| \otimes U_0 + |1\rangle\langle 1| \otimes U_1$$

 Quantum Switch (implementing c-U's with cSWAP's and U's):



  Derive on board: State of the quantum switch at each stage?





Quantum Oracle Using a Quantum Switch

Multiplexing Operator ($N = 2^n$):

$$\text{MUX}_N = \prod_{x \in \{0,1\}^n} |x\rangle\langle x| \otimes U_x$$


If select qubits are $|x\rangle$:
apply U_x to output qubit.

Bit oracle (for NOT function):

  


What initial state should we set for the ancilla?

Quantum Switch:

 

Phase oracle (for NOT function):

 



Quantum Multiplexer

Multiplexing Operator:


$$\text{MUX}_N = \prod_{x \in \{0,1\}^n} |x\rangle\langle x| \otimes U_x$$

If select qubits are $|x\rangle$:
apply U_x to output qubit.

Example (MUX₈):

  


Fanout QRAM

 


Fanout QRAM

Suppose address state is : $\alpha_{010}|010\rangle_a + \alpha_{010}|110\rangle_a$

After address loading:

 

After bus routing:

 


Bucket-Brigade QRAM


Suppose address state is : $\alpha_{010}|010\rangle_a + \alpha_{010}|110\rangle_a$

After address loading:

Introducing “wait” state: $|w\rangle$

 


After bus routing:

 


Quantum Switch on a Three-Level System


Quantum Switch (with wait):

 


$$x \in \{0, 1, w\}$$

 

$$|0\rangle\langle 0| \otimes \text{SWAP}_{\text{out}, \text{in}_0}$$

 

$$|1\rangle\langle 1| \otimes \text{SWAP}_{\text{out}, \text{in}_1}$$

 


$$|w\rangle\langle w| \otimes I$$


Qutrit: $\{|0\rangle, |1\rangle, |2\rangle\}$

2-Qubits: $\{|10\rangle, |01\rangle, |00\rangle\}$

Bucket-Brigade QRAM

 

Suppose $|x_0x_1x_2\rangle = |010\rangle$

 

Derive on board:

- Total qubits?
- Total depth?