

Lecture 10 CPSC 447/547 - Intro to QC

Reversible Logic and Oracles.


Outline

- Quantum query model
- Types of oracles
- Reversible circuits, ancilla & garbage qubits.

How to compute classical Boolean functions on a quantum computer?

Query mode!

Classical:

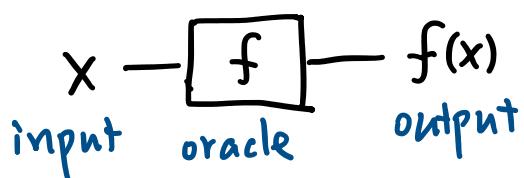


E.g. $f: \{0,1\} \rightarrow \{0,1\}$

$$x \longrightarrow f(x) = \neg x$$


"NOT function"

Quantum:

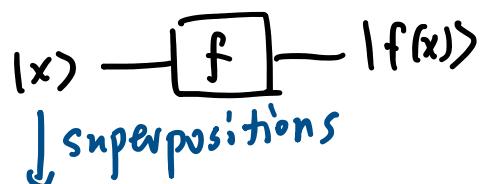

E.g. Same NOT function

$$\alpha|0\rangle + \beta|1\rangle \rightarrow \alpha|f(0)\rangle + \beta|f(1)\rangle$$

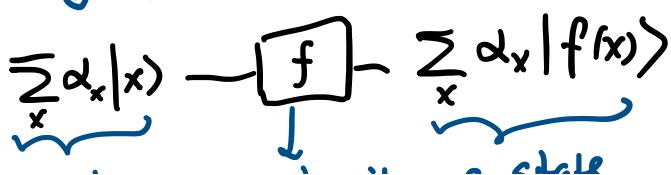

"X gate" $= \alpha|1\rangle + \beta|0\rangle$

q. state q. circuit q. circ

This is like a **query** to some memory
where x is the **address**, and $f(x)$ is the **data**.
but the key here is we can:

"access memory"/"evaluate f " in superposition.


To accomplish this, \boxed{f} must be a **q. circuit**.
(reversible)

Recall from an earlier lecture:

Thm Any Boolean functions $f: \{0,1\}^m \rightarrow \{0,1\}^n$
can be computed by a **reversible circuit**
if k bits input and k bits output, $k \geq m, n$.


Let's see how to do that for general f .

$$f: \{0,1\}^m \rightarrow \{0,1\}^n$$

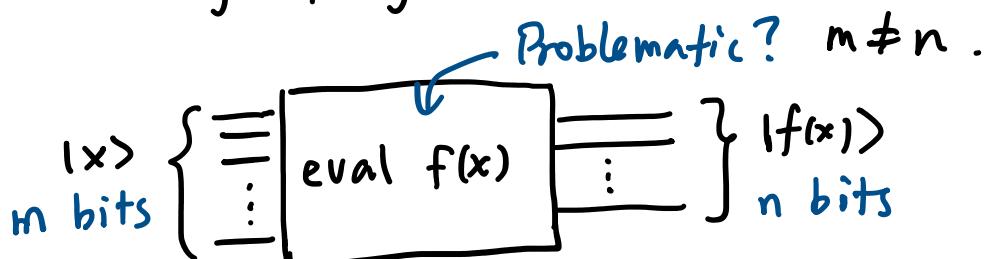

We can fix the mismatch of input/output:

"Bit oracle" (XOR oracle) O_f

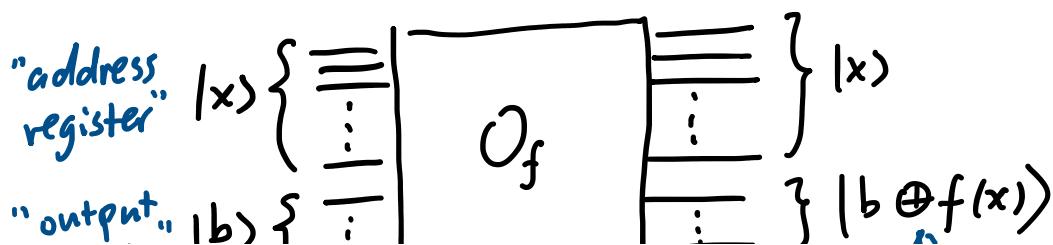


register $|x\rangle$  \rightarrow bitwise $x \oplus b$.

Key: Storing $f(x)$ **out-of-place**.


When $|b\rangle = |0\rangle$, then $|x\rangle|0\rangle \xrightarrow{O_f} |x\rangle|f(x)\rangle$

Remark: with superposition: $\sum_x \alpha_x |x\rangle|0\rangle \xrightarrow{O_f} \sum_x \alpha_x |x\rangle|f(x)\rangle$.

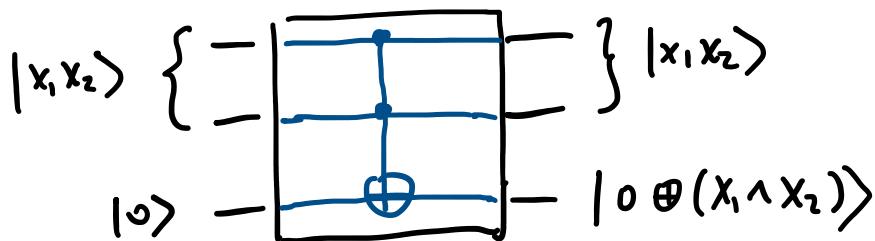E.g.: $f = \text{AND} : \{0,1\}^2 \rightarrow \{0,1\}$



"Phase oracle" O_f^\pm (for $n=1$)

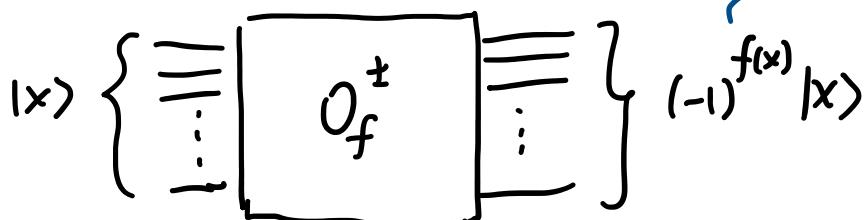


Is this global phase?

Not if we put
in superposition.


Key: Storing output **in the phase**.

Remark: Superposition: $\sum_x \alpha_x |x\rangle \xrightarrow{O_f^\pm} \sum_x \alpha_x (-1)^{f(x)} |x\rangle$.

E.g.: Again for **AND**:

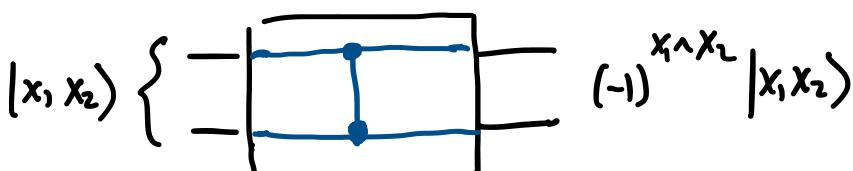

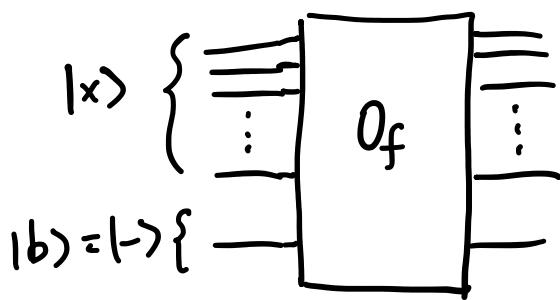Bonus: We can use O_f to implement O_f^\pm



Input :

$$|x>|-> = \frac{1}{\sqrt{2}}(|x>|0> - |x>|1>)$$

? Output :

$$\frac{1}{\sqrt{2}}(|x>|f(x)> - |x>|1 \oplus f(x)>)$$

If $f(x) = 0$:


$$\frac{1}{\sqrt{2}}(|x>|0> - |x>|1>) = |x>|->$$

If $f(x) = 1$:

$$\frac{1}{\sqrt{2}}(|x>|1> - |x>|0>) = (-1)|x>|->$$

$$\left(\sum_x \alpha_x |x> \right) |-> \xrightarrow{O_f} \left(\sum_x \alpha_x (-1)^{f(x)} |x> \right) |->$$

So in the AND example :

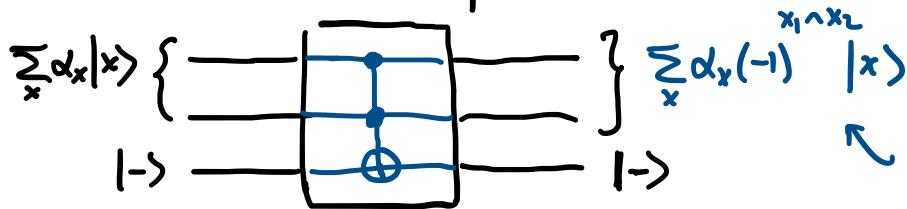

↑ seem to change
the control qubits !

Phase kickback - a closer look .

$$\begin{array}{ccc} \sum_x \alpha_x |x> & \xrightarrow{\text{?}} & \sum_x \alpha_x (-1)^x |x> \\ |-> & \xrightarrow{\oplus} & |-> \end{array}$$

$$(\alpha_0|0> + \alpha_1|1>) \otimes \left(\frac{1}{\sqrt{2}}|0> - \frac{1}{\sqrt{2}}|1> \right) = \frac{\alpha_0}{\sqrt{2}}|00> - \frac{\alpha_0}{\sqrt{2}}|01> + \frac{\alpha_1}{\sqrt{2}}|10> - \frac{\alpha_1}{\sqrt{2}}|11>$$

↓ CNOT

$$\frac{\alpha_0}{\sqrt{2}}|00> - \frac{\alpha_0}{\sqrt{2}}|01> + \frac{\alpha_1}{\sqrt{2}}|11> - \frac{\alpha_1}{\sqrt{2}}|10>$$

$$= \underbrace{(\alpha_0|0> - \alpha_1|1>)}_{\text{Phase kickback}} \otimes \left(\frac{1}{\sqrt{2}}|0> - \frac{1}{\sqrt{2}}|1> \right)$$

Control qubit got a phase!

Let's come back to this idea of using scratch space.

We need scratch space by counting argument.


$$\left\{ \begin{array}{l} \# \text{ functions on } n\text{-bit input, } n\text{-bit output} = (2^n)^{2^n} \\ \# \text{ reversible functions on } n \text{ bits} = (2^n)! \\ \hookrightarrow \text{can be viewed as permutations} \end{array} \right.$$

- Reversible function is a small fraction.


$$\frac{(2^n)!}{(2^n)^{2^n}} \approx \frac{(2^n/e)^{2^n}}{(2^n)^{2^n}} = e^{-2^n}$$

- Reversible function on $(n+1)$ bits $= (2^{n+1})! > (2^n)^{2^n}$

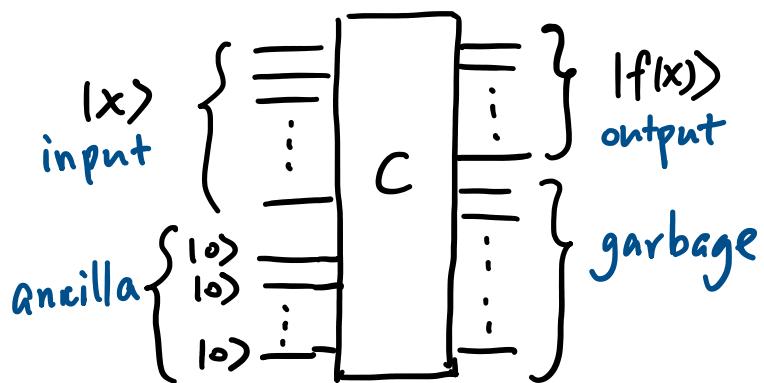
{ How much scratch space do we need?
How to save qubits by reusing ancilla?



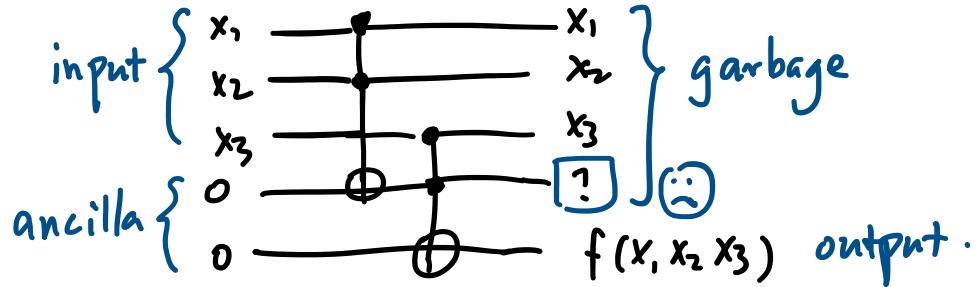
Example for $f = \text{AND}(x_1, x_2, x_3)$.



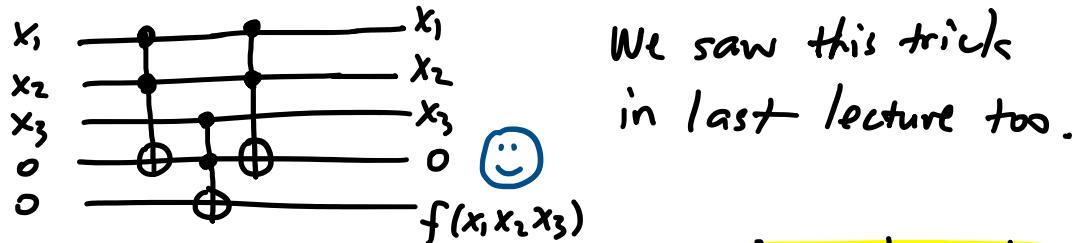Fortunately, some of the garbage bits can be **cleaned up**.



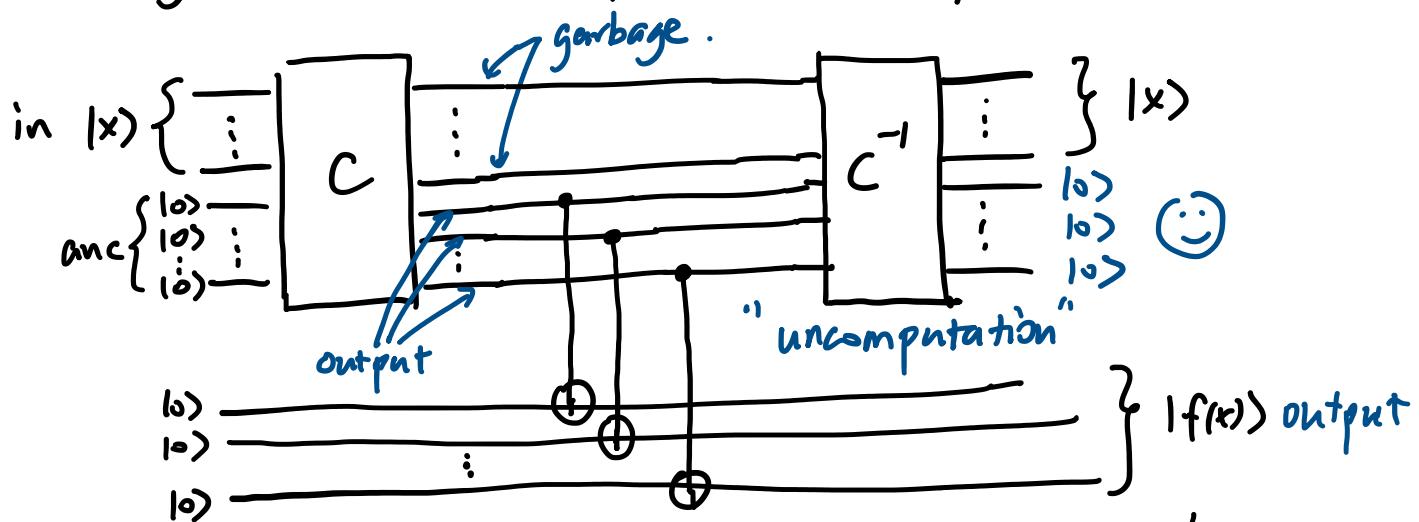In general, we can perform **uncomputation strategies**.



This seems to have **large overhead** though!

We need to run computation C forward and backward.
which means roughly twice as long circuit!


We can do much better !

Divide-and-Conquer (reversible pebble game) Optional

Idea: Clean up garbage frequently by uncomputing parts of C .

Outline

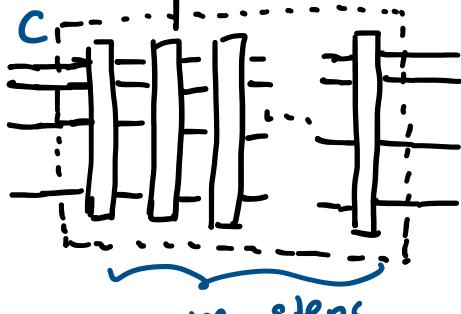
1. Divide computation into m steps . (assume $m=2^d$)



C_0, C_1, \dots, C_{m-1}

(Each accumulate 1 unit of garbage)

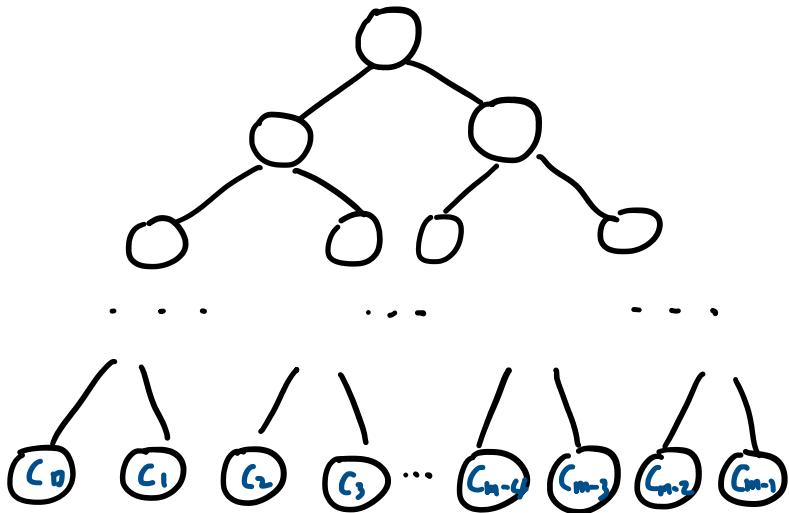2. Construct a balanced binary tree of d layers.



Leaves : computation steps C_i

Branches : $f_p = f_L f_R f_p^{-1}$

3. Run computation according to f_{root} .

- How much garbage accumulated ?
- How long does f_{root} take ?

} D&C § 6.4.3.